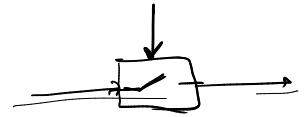


2 transistors \rightarrow NAND.

(Transistors —
electronic switch



NAND	T	F
T	F	T
F	T	T

Claim: NAND is universal, i.e. we can build anything out of NAND.

Lemma: AND+OR+NOT are universal.

Proof:

Lemma: we can build AND, OR, NOT out of NAND.

Proof: Project 1.

Suppose we have an arbitrary Boolean function f .

x	y	$f(x,y)$ — XOR
T	T	F
T	F	T
F	T	T
F	F	F

① Write down the inputs for each row that is T using AND, NOT.

$$x \wedge \neg y$$

$$\neg x \wedge y$$



② Combine with OR:


$$(x \wedge \neg y) \vee (\neg x \wedge y)$$

Let's build XOR gate!

① Come up w/ a boolean expression

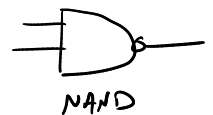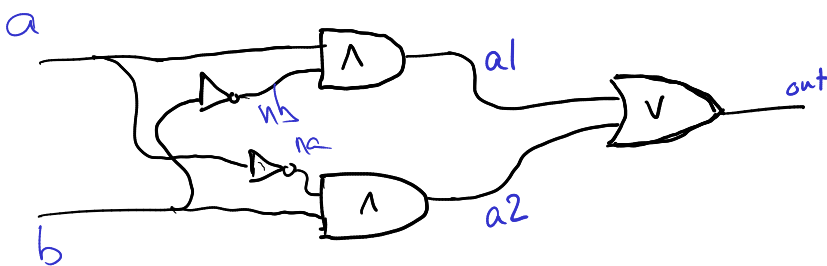
② Draw it as a digital logic circuit diagram.



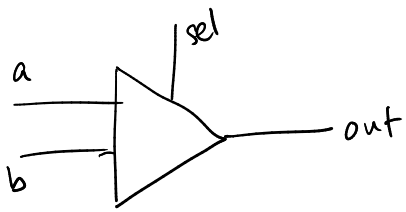

Mux

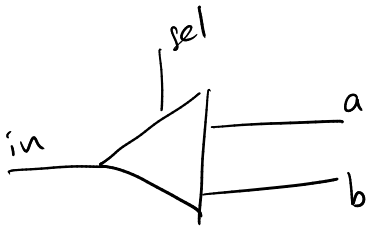either a or b is copied to output depending on sel.



DMux

